

الاسم:
الرقم:

مسابقة في مادة الفيزياء
المدة: ساعة واحدة

This exam is formed of four obligatory exercises in two pages.
Non programmable calculators are allowed

Exercise 1: (4 points) True or False


For each of the following statements, answer by true or false and rewrite the false statements correctly.

- 1) The resistance R_{eq} of the resistor equivalent to two resistors of resistances R_1 and R_2 connected in parallel is: $R_{eq} = R_1 + R_2$.
- 2) The resistance of a resistor is measured by a voltmeter.
- 3) Joule's effect is the transformation of electric energy into heat.
- 4) The effective voltage between the live line and the neutral of the wall outlet is about 220 V.

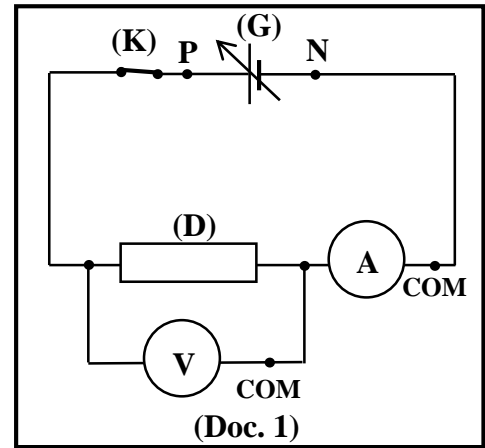Exercise 2: (6 points) Energy consumed by an electric component

Consider the circuit of document 1 that consists of the following components:

- a DC generator (G) of adjustable voltage;
- an electric component (D);
- an ammeter (A);
- a voltmeter (V);
- connecting wires;
- a switch (K).



- 1) We vary the voltage delivered by (G) from 0 to 10 V.
We record the values of U and I displayed respectively by (V) and (A). The results are shown in the table below:


| | | | | | |
|---------------|---|----|----|----|----|
| U (V) | 0 | 2 | 4 | 6 | 10 |
| I (mA) | 0 | 10 | 20 | 30 | 50 |

- 1.1) Draw the characteristic current-voltage curve of (D).
Scale: on the horizontal axis: 1 cm for 10 mA;
on the vertical axis: 1 cm for 2 V.
- 1.2) (D) is a resistor. Justify.
- 1.3) Deduce its resistance R .
- 2) For a voltage, across (D), $U = 8$ V:
 - 2.1) give graphically the corresponding value of I ;
 - 2.2) show that the electric power consumed by (D) is $P = 0.32$ W;
 - 2.3) calculate, in J, the electric energy E consumed by (D) during 10 minutes of functioning.

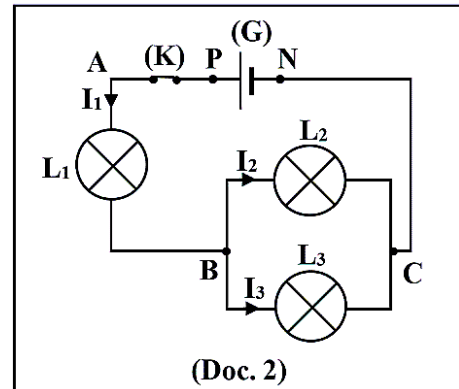Exercise 3: (4 points)**Study of an electric circuit**

The electric circuit of document 2 is formed of:

- a generator (G) that maintains across its terminals a constant voltage $U_{PN} = 9 \text{ V}$;
- three lamps (L_1), (L_2) and (L_3);
- a switch (K);
- connecting wires.




- 1) The switch (K) is closed.
The voltage across (L_1) is $U_{AB} = 3 \text{ V}$.
 - 1.1) Knowing that $U_{PA} = 0 \text{ V}$ and $U_{CN} = 0 \text{ V}$, determine the voltage U_{BC} .
 - 1.2) Deduce, by indicating the law used, the voltage across the terminals of (L_2) and that across the terminals of (L_3).
 - 1.3) The generator sends a current $I_1 = 500 \text{ mA}$.
The current through (L_2) is $I_2 = 300 \text{ mA}$.
Determine the current I_3 through (L_3).
- 2) The switch (K) is open.
Give the new values of U_{PA} and U_{BC} .

Exercise 4: (6 points)**Alternating Sinusoidal Voltage**

Document 3 represents the waveform of an alternating sinusoidal voltage (u) delivered by a low frequency generator (LFG).

In the absence of any voltage, the horizontal luminous line passes through the center of the screen of the oscilloscope.


- 1) Knowing that the frequency f of (u) is 50 Hz :
 - 1.1) show that its period T is 20 ms ;
 - 1.2) deduce the horizontal sensitivity S_h of the oscilloscope.
- 2) The vertical sensitivity S_v of the oscilloscope is adjusted to 5 V/div .
Referring to document 3, calculate the maximum value U_m of (u).
- 3) A voltmeter, in the AC mode, connected across this generator indicates a value U .
 - 3.1) What does U represent?
 - 3.2) Calculate its value.
- 4) A lamp (L) acting as a resistor and carries the inscription 12 V is connected across this generator.
 - 4.1) Give the significance of the inscription 12 V .
 - 4.2) (L) glows normally. Justify.

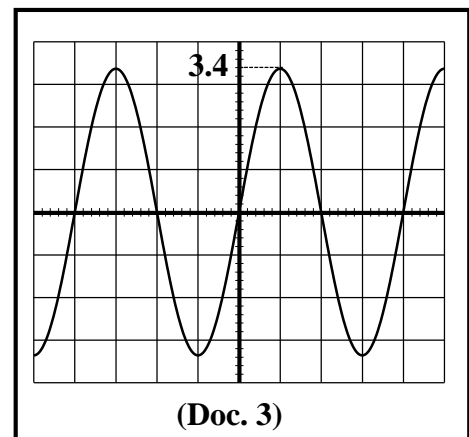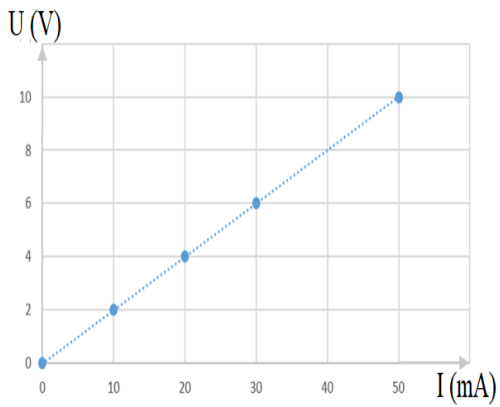

Exercise 1: (4 points) True or false

| Question | Answer | Mark |
|----------|---|------|
| 1 | False. The resistance R_{eq} of the resistor equivalent to two resistors of resistances R_1 and R_2 connected in serie is: $R_{eq} = R_1 + R_2$. Or: The resistance R_{eq} of the resistor equivalent to two resistors of resistances R_1 and R_2 connected in parallel is: $R_{eq} = \frac{R_1 \times R_2}{R_1 + R_2}$ | 1 |
| 2 | False. The resistance of a resistor can be measured by an ohmmeter. | 1 |
| 3 | True. | 1 |
| 4 | True. | 1 |

Exercise 2: (6 points) Energy consumed by an electric component

| Question | Answer | Mark |
|----------|--|------|
| 1.1 |  | 1 |
| 1.2 | Since its characteristic curve is a straight line passing through O. | 1 |
| 1.3 | for $I = 10 \text{ mA}$, $U = 2 \text{ V}$, therefore $R = \frac{U}{I} = \frac{2\text{V}}{0.01\text{A}} = 200 \Omega$ (Ohm's law). | 1.25 |
| 2.1 | $I = 40\text{mA} = 0.04 \text{ A}$ (graph) | 0.5 |
| 2.2 | $P = U \times I = 8 \times 0.04 = 0.32 \text{ W}$ | 1 |
| 2.3 | $E = P \times t = 0.32 \times 10 \times 60 = 192 \text{ J}$. | 1.25 |

Exercise 3: (4 points) Study of an electric circuit

| Question | Answer | Mark |
|------------|---|--------------------------|
| 1.1 | $U_{BC} = U_{BA} + U_{AP} + U_{PN} + U_{NC}$ (law of addition of voltages) $U_{BC} = -3 + 0 + 9 + 0 = 6 \text{ V}$. | 1 |
| 1.2 | $U_2 = U_3 = 6 \text{ V}$ (law of uniqueness of voltage in parallel). | 1 |
| 1.3 | $I_3 = I_1 - I_2 = 500 - 300 = 200 \text{ mA}$ (law of addition of currents) | 1 |
| 2 | $U_{PA} = U_{PN} = 9 \text{ V}$. $U_{BC} = 0 \text{ V}$. | 0.5 0.5 |

Exercise 4: (6 points) Alternating Sinusoidal Voltage

| Question | Answer | Mark |
|------------|---|------------|
| 1.1 | $T = 1/f = 1/50 = 0.02 \text{ s} = 20 \text{ ms}$. | 1 |
| 1.2 | $S_h = T/x = 20\text{ms} / 4 \text{ divisions} = 5 \text{ ms/div}$. | 1 |
| 2 | $U_m = S_v \times y_m = 3.4 \times 5 = 17 \text{ V}$. | 1 |
| 3.1 | It's the effective voltage. | 0.5 |
| 3.2 | $U = U_m / \sqrt{2} = 17 / \sqrt{2} = 12.02 \text{ V}$. | 1 |
| 4.1 | 12 V represent the rated voltage of the lamp. | 0.5 |
| 4.2 | This lamp functions normally since its rated voltage is (almost) equal to the effective voltage of the generator. | 1 |